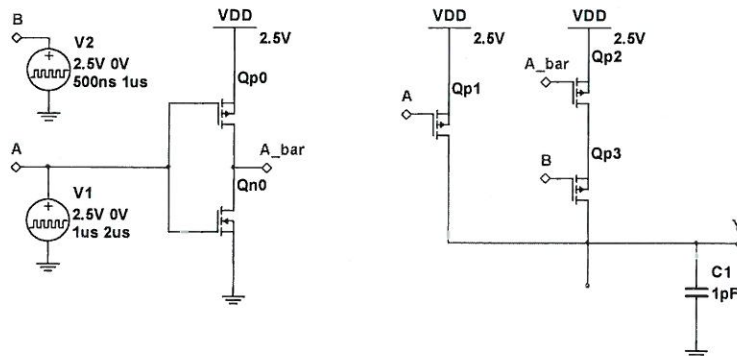


Name _____

Section _____

1. (100 points) The figure below shows the pull-up network (PUN) for a logic function Y with 3 inputs.




a. (25 points) Fill in the truth table below.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

b. (25 points) Determine the logic function for Y, either by inspection or reducing the truth table.

$$Y = \bar{A} + A\bar{B} = \bar{A} + \bar{B} = \overline{AB}$$

 c. (25 points) Draw the pull-down network (PDN).




d. (25 points) If an inverter with $\left(\frac{W}{L}\right)_n = \frac{90 \text{ nm}}{45 \text{ nm}}$ and $\left(\frac{W}{L}\right)_p = \frac{225 \text{ nm}}{45 \text{ nm}}$ produces equal t_{PHL} and t_{PLH} , and we want to match those delays with our gate, size the transistors in the pull-up network. The minimum-length transistors have channel length, L , of 45 nm.

$$\left(\frac{W}{L}\right)_{QP1} = \frac{225 \text{ nm}}{45 \text{ nm}} \quad \left(\frac{W}{L}\right)_{QP2} = \frac{450}{45} \quad \left(\frac{W}{L}\right)_{QP3} = \frac{450}{45}$$

Bonus. (Up to 25 points) Minimize the expression for \bar{Y} and draw the pull-up network to implement the minimized expression. Size the transistors for worst-case delay to match the delay of the reference inverter.

$$Y = \bar{A} + \bar{B}$$
 
$$\bar{Y} = \overline{\bar{A} + \bar{B}} = AB$$



2. (100 points) Figures 2 and 3 below show two different options to implement the PDN from Part I whose logic function Y was $Y = \bar{A} + A\bar{B}$, with PUN shown in Figure 1.

 


Figure 1 PUN

 


Figure 2 PDN option 1

 


Figure 3 PDN option 2

- (10 points) Write the logic function \bar{Y} for PDN option 1. Do not reduce.

$$\bar{Y} = A(B + \bar{A})$$

- (10 points) Write the logic function \bar{Y} for PDN option 2. Do not reduce.

$$\bar{Y} = AB + A\bar{A}$$

- (10 points) Write the minimized logic function of \bar{Y} and draw the PDN to the right.

$$\bar{Y} = AB$$

- (25 points) What is the sizing requirement $n = x(W/L)$ for each PDN transistor in options 1 and 2 and in the minimized PDN. x is the factor by which the basic inverter is scaled.

$x\text{-option 1} = \underline{2}$ (3x each)
 $x\text{-option 2} = \underline{2}$ (4x each)
 $x\text{-minimized} = \underline{2}$ (2x each)

- (45 points) Using your results above, explain why using reduced logic functions reduces the area required to synthesize a logic function, while optimizing delays.

we gain nothing in sizing by using a non-minimized implementation and it takes more transistors (per transistor)