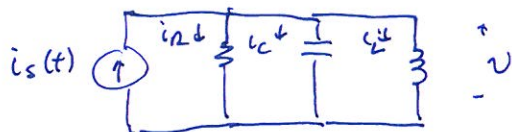


ECE332 Quiz 2
(10 minutes)

Name: _____

1. [50 pts] **Given:** A parallel RLC circuit with a Norton current source. Assume an ideal inductor and an ideal current source i.e. no parasitic resistance and source resistance $R_S = \infty$.

[20 pts] **Find:** Develop the ODE using connection constraints (KVL and/or KCL) and i-v relationships with appropriate substitutions. Do not solve.



$$i_R + i_C + i_L = i_s$$

$$i_R = \frac{v}{R} = \frac{L \dot{i}_L}{R}$$

$$i_C = C v_C' = \frac{CL}{R} \ddot{i}_L$$

$$LC \ddot{i}_L + \frac{L}{R} \dot{i}_L + i_L = i_s$$

$$\ddot{i}_L + \frac{1}{RC} \dot{i}_L + \frac{1}{LC} i_L = \frac{1}{LC} i_s$$

- [10 pts] **Find:** The characteristic equation in terms of R, L, and C.

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

- [10 pts] **Find:** The roots of the characteristic equation in terms of R, L, and C.

$$s = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

- [10 pts] **Find:** Given that the roots above are complex, explain whether increasing R makes your circuit **more** or **less** damped.

increasing R makes determinant closer to $\frac{1}{LC} \Rightarrow$ decreases ζ

2. [50 pts] **Given:** Assume you found the characteristic equation from above to be

$$s^2 + \frac{1}{RC}s + \frac{1}{LC}$$

$$s^2 + 2\zeta\omega_0 s + \omega_0^2$$

alternative form

- a. [10 pts] **Find:** Using the alternative form of the characteristic equation, find the undamped natural frequency ω_0 strictly in terms of R, L, and/or C.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- b. [20 pts] **Find:** Using the alternative form of the characteristic equation, find the damping factor ζ in terms of R, L, and/or C.

$$2\zeta\omega_0 = \frac{1}{RC}$$

$$2\zeta \frac{1}{\sqrt{LC}} = \frac{1}{RC}$$

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

- c. [20 pts] **Find:** Determine R, L, and/or C for $\zeta = 0.25$. Standard parts are not required.

ω_0 not given \Rightarrow 2 degrees of freedom

Choose $L = 1 \text{ mH}$
 $C = 0.01 \mu\text{F}$

$$0.25 = \frac{1}{2R} \sqrt{\frac{1\text{m}}{0.01\mu}} \quad R = \frac{1}{2(0.25)} \sqrt{\frac{1\text{m}}{0.01\mu}} = 632 \Omega$$