


ECE 332 Quiz 5
(10 minutes)

Name: _____

1. [100 pts] **Given:** The transfer function below.

$$T(s) = \frac{\pm 50000s}{(s + 50)(s + 1000)}$$

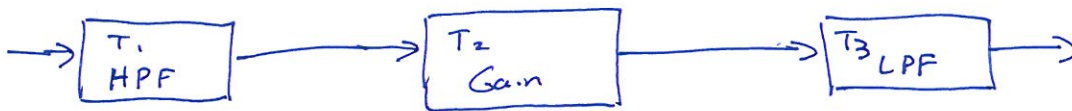- a. [30 pts] **Find:** Rewrite $T(s)$ as a cascaded connection of 3 stages. Use two passive 1st-order filter stages and one gain stage. Clearly label each stage.



$$T_1(s) = \frac{s}{s+50}$$


$$T_2(s) = 50$$

$$T_3(s) = \frac{1000}{s+1000}$$

- b. [10 pts] **Find:** Based on how you cascaded $T(s)$ in part a, what filter function does it perform?

Bandpass filter

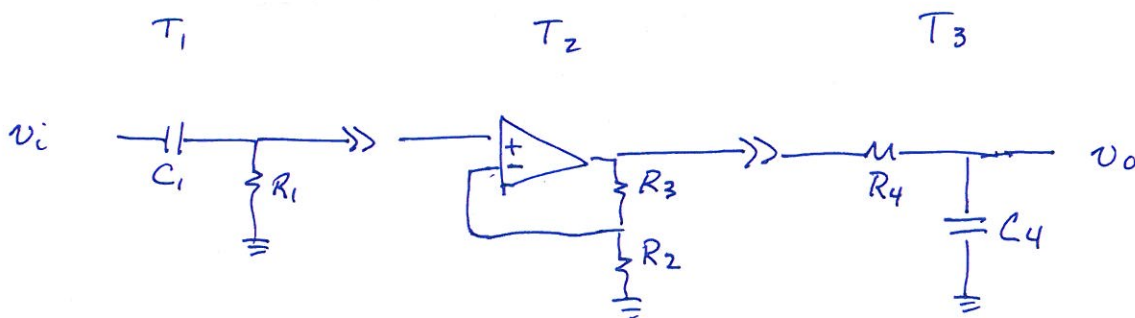- c. [40 pts] **Find:** Draw a circuit below to realize $T(s)$ using only resistors, capacitors, and OP AMP(s). Do not select resistor and capacitor values at this time. Ensure you consider loading. Clearly label each stage according to part a.



d. [10 pts] **Find:** What are the corner frequencies of $T(s)$ i.e. the poles?

$$\omega_{cl} = 50 \text{ rad/sec} \quad s = -50$$

$$\omega_{ch} = 1000 \text{ rad/sec} \quad s = -1000$$

e. [10 pts] **Find:** Select appropriate values of resistors and capacitors to realize your circuit using only $1 \mu\text{F}$ capacitors.

$$\frac{1}{R_1 C_1} = 50 \quad C_1 = 1.0 \mu\text{F} \quad R_1 = \frac{1}{1\mu \cdot 50} = 20 \text{ k}\Omega$$

$$\frac{1}{R_4 C_4} = 1000 \quad C_4 = 1.0 \mu\text{F} \quad R_4 = \frac{1}{1\mu \cdot 1000} = \frac{1}{1\text{m}} = 1 \text{ k}\Omega$$

$$\text{Gain} = 1 + \frac{R_3}{R_2} = 50 \quad \text{Choose } R_2 = 1 \text{ k}\Omega$$

$$R_3 = 49 R_2 = 49 \text{ k}\Omega$$