

which is 10 times W_1 , as needed to provide $I_{D2} = 10I_{D1}$. Since Q_2 is to operate at the edge of saturation,

$$V_{DS2} = V_{OV}$$


Thus,

$$V_{D2} = 0.25 \text{ V}$$

and

$$\begin{aligned} R_2 &= \frac{V_{DD} - V_{D2}}{I_{D2}} \\ &= \frac{1.8 - 0.25}{0.5} = 3.1 \text{ k}\Omega \end{aligned}$$

5.47

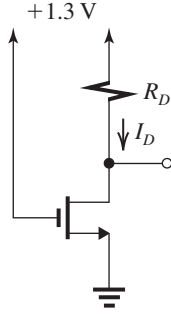

$$\begin{aligned} I_D &= \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} \times 0.4 \times \frac{W}{L} (1.3 - 0.4)^2 \\ &= 0.162 \left(\frac{W}{L} \right) \end{aligned}$$

$$V_D = 1.3 - I_D R_D = 1.3 - 0.162 \left(\frac{W}{L} \right) R_D$$

For the MOSFET to be at the edge of saturation, we must have


$$V_D = V_{OV} = 1.3 - 0.4 = 0.9$$

Thus

$$0.9 = 1.3 - 0.162 \left(\frac{W}{L} \right) R_D$$

$$\Rightarrow \left(\frac{W}{L} \right) R_D \simeq 2.5 \text{ k}\Omega \quad \text{Q.E.D}$$

5.48

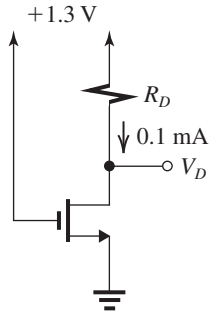

$$\begin{aligned} V_{OV} &= V_{GS} - V_t \\ &= 1.3 - 0.4 = 0.9 \end{aligned}$$


To operate at the edge of saturation, we must have

$$V_D = V_{OV} = 0.9 \text{ V}$$

Thus,

$$R_D = \frac{1.3 - 0.9}{0.1} = 4 \text{ k}\Omega$$

5.49

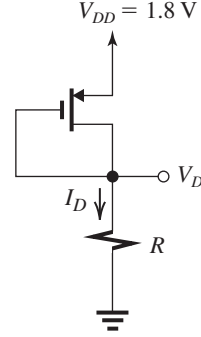

$$I_D = 180 \text{ }\mu\text{A} \quad \text{and} \quad V_D = 1 \text{ V}$$

$$R = \frac{V_D}{I_D} = \frac{1}{0.18} = 5.6 \text{ k}\Omega$$

Transistor is operating in saturation with $|V_{OV}| = 1.8 - V_D - |V_t| = 1.8 - 1 - 0.5 = 0.3 \text{ V}$:

$$I_D = \frac{1}{2} k'_p \frac{W}{L} |V_{OV}|^2$$

$$180 = \frac{1}{2} \times 100 \times \frac{W}{L} \times 0.3^2$$

$$\Rightarrow \frac{W}{L} = 40$$

$$W = 40 \times 0.18 = 7.2 \text{ }\mu\text{m}$$

5.50 Refer to Fig. P5.50. Both Q_1 and Q_2 are operating in saturation at $I_D = 0.5 \text{ mA}$. For Q_1 ,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} V_{OV1}^2$$

$$0.5 = \frac{1}{2} \times 0.25 \times \frac{W_1}{L_1} (1 - 0.5)^2$$

$$\Rightarrow \frac{W_1}{L_1} = 16$$

$$W_1 = 16 \times 0.25 = 4 \text{ }\mu\text{m}$$

For Q_2 , we have

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W_2}{L_2} \right) V_{OV2}^2$$

$$0.5 = \frac{1}{2} \times 0.25 \times \frac{W_2}{L_2} (1.8 - 1 - 0.5)^2$$

$$\Rightarrow \frac{W_2}{L_2} = 44.4$$

$$W_2 = 44.4 \times 0.25 = 11.1$$

$$R = \frac{2.5 - 1.8}{0.5} = 1.4 \text{ k}\Omega$$

5.51 Refer to the circuit in Fig. P5.51. All three transistors are operating in saturation with $I_D = 90 \mu\text{A}$. For Q_1 ,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{GS1} - V_t)^2$$

$$90 = \frac{1}{2} \times 90 \times \frac{W_1}{L_1} (0.8 - 0.5)^2$$

$$\Rightarrow \frac{W_1}{L_1} = 22.2$$

$$W_1 = 22.2 \times 0.5 = 11.1 \mu\text{m}$$

For Q_2 ,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W_2}{L_2} (V_{GS2} - V_t)^2$$

$$90 = \frac{1}{2} \times 90 \times \frac{W_2}{L_2} (1.5 - 0.8 - 0.5)^2$$

$$\Rightarrow \frac{W_2}{L_2} = 50$$

$$W_2 = 50 \times 0.5 = 25 \mu\text{m}$$

For Q_3 ,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W_3}{L_3} (V_{GS3} - V_t)^2$$

$$90 = \frac{1}{2} \times 90 \times \frac{W_3}{L_3} (2.5 - 1.5 - 0.5)^2$$

$$\Rightarrow \frac{W_3}{L_3} = 8$$

$$W_3 = 8 \times 0.5 = 4 \mu\text{m}$$

5.52 Refer to the circuits in Fig. 5.24 (page 282):

$$V_{GS} = 5 - 6I_D$$

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 1.5 \times (5 - 6I_D - 1.5)^2$$

which results in the following quadratic equation in I_D :

$$36I_D^2 - 43.33I_D + 12.25 = 0$$

The physically meaningful root is


$$I_D = 0.45 \text{ mA}$$

This should be compared to the value of 0.5 mA found in Example 5.6. The difference of about 10% is relatively small, given the large variations in k_n and V_t (50% increase in each). The new value of V_D is

$$V_D = V_{DD} - R_D I_D = 10 - 6 \times 0.45 = +7.3 \text{ V}$$

as compared to +7 V found in Example 5.6. We conclude that this circuit is quite tolerant to variations in device parameters.

5.53

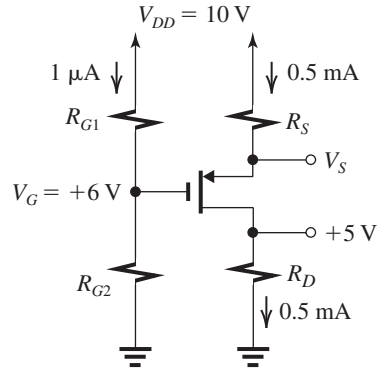

Refer to the circuit in the figure above,

$$R_{G1} = \frac{V_{DD} - V_G}{1 \mu\text{A}}$$

$$= \frac{10 - 6}{1} = 4 \text{ M}\Omega$$

$$R_{G2} = \frac{6}{1 \mu\text{A}} = 6 \text{ M}\Omega$$

$$R_D = \frac{5 \text{ V}}{0.5 \text{ mA}} = 10 \text{ k}\Omega$$

To determine V_S , we use

$$I_D = \frac{1}{2} k'_p \left(\frac{W}{L} \right) (V_{SG} - |V_t|)^2$$

$$0.5 = \frac{1}{2} \times 4 \times (V_{SG} - 1.5)^2$$

$$\Rightarrow V_{SG} = 2 \text{ V}$$

Thus,

$$V_S = V_G + V_{SG} = 6 + 2 = 8 \text{ V}$$

$$R_S = \frac{10 - 8}{0.5} = 4 \text{ k}\Omega$$

7.1 Coordinates of point A: $v_{GS} = V_t = 0.5$ V and $v_{DS} = V_{DD} = 5$ V.

To obtain the coordinates of point B, we first use Eq. (7.6) to determine $V_{GS}|_B$ as

$$\begin{aligned} V_{GS}|_B &= V_t + \frac{\sqrt{2k_n R_D V_{DD} + 1} - 1}{k_n R_D} \\ &= 0.5 + \frac{\sqrt{2 \times 10 \times 20 \times 5 + 1} - 1}{10 \times 20} \\ &= 0.5 + 0.22 = 0.72 \text{ V} \end{aligned}$$

The vertical coordinate of point B is $V_{DS}|_B$,

$$V_{DS}|_B = V_{GS}|_B - V_t = V_{OV}|_B = 0.22 \text{ V}$$

7.2 $V_{DS}|_B = V_{OV}|_B = 0.5$ V

Thus,

$$I_D|_B = \frac{1}{2} k_n V_{DS}^2|_B = \frac{1}{2} \times 5 \times 0.5^2 = 0.625 \text{ mA}$$

The value of R_D required can now be found as

$$\begin{aligned} R_D &= \frac{V_{DD} - V_{DS}|_B}{I_D|_B} \\ &= \frac{5 - 0.5}{0.625} = 7.2 \text{ k}\Omega \end{aligned}$$

If the transistor is replaced with another having twice the value of k_n , then $I_D|_B$ will be twice as large and the required value of R_D will be half that used before, that is, 3.6 k Ω .

7.3 Bias point Q: $V_{OV} = 0.2$ V and $V_{DS} = 1$ V.

$$\begin{aligned} I_{DQ} &= \frac{1}{2} k_n V_{OV}^2 \\ &= \frac{1}{2} \times 10 \times 0.04 = 0.2 \text{ mA} \\ R_D &= \frac{V_{DD} - V_{DS}}{I_{DQ}} = \frac{5 - 1}{0.2} = 20 \text{ k}\Omega \end{aligned}$$

Coordinates of point B:

Equation (7.6):

$$\begin{aligned} V_{GS}|_B &= V_t + \frac{\sqrt{2k_n R_D V_{DD} + 1} - 1}{k_n R_D} \\ &= 0.5 + \frac{\sqrt{2 \times 10 \times 20 \times 5 + 1} - 1}{10 \times 20} \\ &= 0.5 + 0.22 = 0.72 \text{ V} \end{aligned}$$

Equations (7.7) and (7.8):

$$\begin{aligned} V_{DS}|_B &= \frac{\sqrt{2k_n R_D V_{DD} + 1} - 1}{k_n R_D} = 0.22 \text{ V} \\ A_v &= -k_n R_D V_{OV} \\ &= -10 \times 20 \times 0.2 = -40 \text{ V/V} \end{aligned}$$

The lowest instantaneous voltage allowed at the output is $V_{DS}|_B = 0.22$ V. Thus the maximum allowable negative signal swing at the output is $V_{DSQ} - 0.22 = 1 - 0.22 = 0.78$ V. The corresponding peak input signal is

$$\hat{v}_{gs} = \frac{0.78 \text{ V}}{|A_v|} = \frac{0.78}{40} = 19.5 \text{ mV}$$

7.4 From Eq. (7.18):

$$|A_{v \max}| = \frac{V_{DD} - V_{OV}|_B}{V_{OV}|_B/2}$$

$$14 = \frac{2 - V_{OV}|_B}{V_{OV}|_B/2}$$

$$\Rightarrow V_{OV}|_B = 0.25 \text{ V}$$

Now, using Eq. (7.15) at point B, we have

$$A_v|_B = -k_n V_{OV}|_B R_D$$

Thus,

$$\begin{aligned} -14 &= -k_n R_D \times 0.25 \\ \Rightarrow k_n R_D &= 56 \end{aligned}$$

To obtain a gain of -12 V/V at point Q:

$$\begin{aligned} -12 &= -k_n R_D V_{OV}|_Q \\ &= -56 V_{OV}|_Q \end{aligned}$$


Thus,

$$V_{OV}|_Q = \frac{12}{56} = 0.214 \text{ V}$$

To obtain the required $V_{DS}|_Q$, we use Eq. (7.17),

$$\begin{aligned} A_v &= -\frac{V_{DD} - V_{DS}|_Q}{V_{OV}|_Q/2} \\ -12 &= -\frac{2 - V_{DS}|_Q}{0.214/2} \\ \Rightarrow V_{DS}|_Q &= 0.714 \text{ V} \end{aligned}$$

7.5

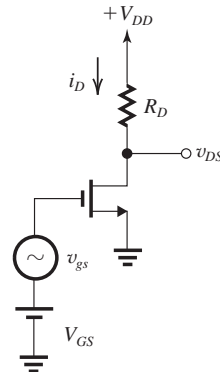

$$V_{DD} = 5 \text{ V}, \quad k'_n \frac{W}{L} = 1 \frac{\text{mA}}{\text{V}^2}$$

$$R_D = 24 \text{ k}\Omega, \quad V_t = 1 \text{ V}$$

(a) Endpoints of saturation transfer segment:

Point A occurs at $V_{GS} = V_t = 1 \text{ V}, i_D = 0$

Point A = (1 V, 5 V) (V_{GS}, V_{DS})

Point B occurs at sat/triode boundary ($V_{GD} = V_t$)

$$V_{GD} = 1 \text{ V} \Rightarrow V_{GS} - [5 - i_D R_D] = 1$$

$$V_{GS} - 5 + \left(\frac{1}{2}\right)(1)(24)[V_{GS} - 1]^2 - 1 = 0$$

$$12V_{GS}^2 - 23V_{GS} + 6 = 0$$

$$V_{GS} = 1.605 \text{ V}$$

$$i_D = 0.183 \text{ mA} \quad V_{DS} = 0.608 \text{ V}$$

Point B = (+1.61 V, 0.61 V)

(b) For $V_{OV} = V_{GS} - V_t = 0.5 \text{ V}$, we have

$$V_{GS} = 1.5 \text{ V}$$

$$I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 1(1.5 - 1)^2$$

$$I_D = 0.125 \text{ mA} \quad V_{DS} = +2.00 \text{ V}$$

Point Q = (1.50 V, 2.00 V)

$$A_v = -k_n V_{OV} R_D = -12 \text{ V/V}$$

(c) From part (a) above, the maximum instantaneous input signal while the transistor remains in saturation is 1.61 V and the corresponding output voltage is 0.61 V. Thus, the maximum amplitude of input sine wave is $(1.61 - 1.5) = 0.11 \text{ V}$. That is, v_{GS} ranges from $1.5 - 0.11 = 1.39 \text{ V}$, at which

$$i_D = \frac{1}{2} \times 1 \times (1.39 - 1)^2 = 0.076 \text{ mA}$$

and

$$v_{DS} = 5 - 0.076 \times 24 = 3.175 \text{ V}$$

and $v_{GS} = 1.5 + 0.11 = 1.61 \text{ V}$ at which

$$v_{DS} = 0.61 \text{ V}.$$

Thus, the large-signal gain is

$$\frac{0.61 - 3.175}{1.61 - 1.39} = -11.7 \text{ V/V}$$

whose magnitude is slightly less (-2.5%) than the incremental or small-signal gain (-12 V/V).

This is an indication that the transfer characteristic is not a straight line.

$$7.6 \quad R_D = 20 \text{ k}\Omega$$

$$k'_n = 200 \mu\text{A/V}^2$$

$$V_{RD} = 1.5 \text{ V}$$

$$V_{GS} = 0.7 \text{ V}$$

$$A_v = -10 \text{ V/V}$$

$$A_v = -k_n V_{OV} R_D$$

$$V_{RD} = I_D R_D = \frac{1}{2} k_n V_{OV}^2 R_D$$

$$\frac{A_v}{V_{RD}} = \frac{-2}{V_{OV}} = \frac{-10}{1.5}$$

$$\therefore V_{OV} = 0.30 \text{ V}$$

$$V_t = V_{GS} - V_{OV} = 0.40 \text{ V}$$

$$k_n = \frac{A_v}{V_{OV} R_D} = \frac{-10}{-0.3 \times 20}$$

$$= 1.67 \text{ mA/V}^2$$

$$k_n = k'_n \frac{W}{L} = 1.67 \text{ mA/V}^2$$

$$\therefore \frac{W}{L} = 8.33$$

7.7 At sat/triode boundary

$$v_{GS}|_B = V_{GS} + \hat{v}_{gs}$$

$$v_{DS}|_B = V_{DS} - \hat{v}_o$$

($\hat{v}_o = \text{max downward amplitude}$), we get

$$v_{DS}|_B = v_{GS}|_B - V_t = V_{GS} + \frac{\hat{v}_o}{|A_v|} - V_t$$

$$= V_{DS} - \hat{v}_o$$

$$V_{OV} + \frac{\hat{v}_o}{|A_v|} = V_{DS} - \hat{v}_o$$

$$\hat{v}_o = \frac{V_{DS} - V_{OV}}{1 + \frac{1}{|A_v|}} \quad (1)$$

For $V_{DD} = 5 \text{ V}, V_{OV} = 0.5 \text{ V}$, and

$$k'_n \frac{W}{L} = 1 \text{ mA/V}^2, \text{ we use}$$

$$A_v = \frac{-2(V_{DD} - V_{DS})}{V_{OV}}$$

and Eq. (1) to obtain

V_{DS}	A_v	\hat{v}_o	\hat{v}_i
1 V	-16	471 mV	29.4 mV
1.5 V	-14	933 mV	66.7 mV
2 V	-12	1385 mV	115 mV
2.5 V	-10	1818 mV	182 mV