

The junction areas of the four diodes must be related by the same ratios as their currents, thus

$$A_4 = 2A_3 = 4A_2 = 8A_1$$

With  $I_1 = 0.1$  mA,

$$I = 0.1 + 0.2 + 0.4 + 0.8 = 1.5 \text{ mA}$$

**4.27** We can write a node equation at the anodes:

$$I_{D2} = I_1 - I_2 = 7 \text{ mA}$$

$$I_{D1} = I_2 = 3 \text{ mA}$$

We can write the following equation for the diode voltages:

$$V = V_{D2} - V_{D1}$$

If  $D_2$  has saturation current  $I_S$ , then  $D_1$ , which is 10 times larger, has saturation current  $10I_S$ . Thus we can write

$$I_{D2} = I_S e^{V_{D2}/V_T}$$

$$I_{D1} = 10I_S e^{V_{D1}/V_T}$$

Taking the ratio of the two equations above, we have

$$\frac{I_{D2}}{I_{D1}} = \frac{7}{3} = \frac{1}{10} e^{(V_{D2}-V_{D1})/V_T} = \frac{1}{10} e^{V/V_T}$$

$$\Rightarrow V = 0.025 \ln\left(\frac{70}{3}\right) = 78.7 \text{ mV}$$

To instead achieve  $V = 60$  mV, we need

$$\frac{I_{D2}}{I_{D1}} = \frac{I_1 - I_2}{I_2} = \frac{1}{10} e^{0.06/0.025} = 1.1$$

Solving the above equation with  $I_1$  still at 10 mA, we find  $I_2 = 4.76$  mA.

**4.28** We can write the following node equation at the diode anodes:

$$I_{D2} = 10 \text{ mA} - V/R$$

$$I_{D1} = V/R$$

We can write the following equation for the diode voltages:

$$V = V_{D2} - V_{D1}$$

We can write the following diode equations:

$$I_{D2} = I_S e^{V_{D2}/V_T}$$

$$I_{D1} = I_S e^{V_{D1}/V_T}$$

Taking the ratio of the two equations above, we have

$$\frac{I_{D2}}{I_{D1}} = \frac{10 \text{ mA} - V/R}{V/R} = e^{(V_{D2}-V_{D1})/V_T} = e^{V/V_T}$$

To achieve  $V = 50$  mV, we need

$$\frac{I_{D2}}{I_{D1}} = \frac{10 \text{ mA} - 0.05/R}{0.05/R} = e^{0.05/0.025} = 7.39$$

Solving the above equation, we have


$$R = 42 \Omega$$

**4.29** For a diode conducting a constant current, the diode voltage decreases by approximately 2 mV per increase of  $1^\circ\text{C}$ .

$T = -20^\circ\text{C}$  corresponds to a temperature decrease of  $40^\circ\text{C}$ , which results in an increase of the diode voltage by 80 mV. Thus  $V_D = 770$  mV.

$T = +85^\circ\text{C}$  corresponds to a temperature increase of  $65^\circ\text{C}$ , which results in a decrease of the diode voltage by 130 mV. Thus  $V_D = 560$  mV.

**4.30**

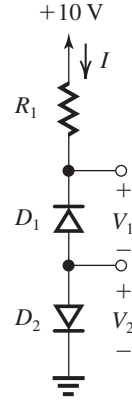


At  $20^\circ\text{C}$ :

$$V_{R1} = V_2 = 520 \text{ mV}$$

$$R_1 = 520 \text{ k}\Omega$$

$$I = \frac{520 \text{ mV}}{520 \text{ k}\Omega} = 1 \mu\text{A}$$

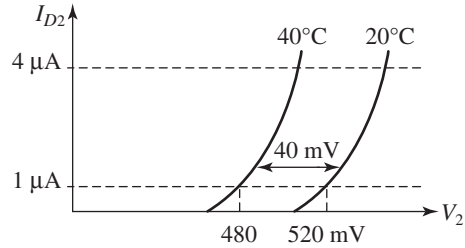Since the reverse current doubles for every  $10^\circ\text{C}$  rise in temperature, at  $40^\circ\text{C}$ ,  $I = 4 \mu\text{A}$



$$V_2 = 480 + 2.3 \times 1 \times 25 \log 4$$

$$= 514.6 \text{ mV}$$

$$V_{R1} = 4 \mu\text{A} \times 520 \text{ k}\Omega = 2.08 \text{ V}$$

$$\text{At } 0^\circ\text{C}, I = \frac{1}{4} \mu\text{A}$$

$$V_2 = 560 - 2.3 \times 1 \times 25 \log 4$$

$$= 525.4 \text{ mV}$$

$$V_{R1} = \frac{1}{4} \times 520 = 0.13 \text{ V}$$

$$= 0.6882 \text{ V}$$

$$4. \ v = 0.7 + 2.3 \times 0.025 \log\left(\frac{0.6235}{1}\right)$$

$$= 0.6882 \text{ V}$$

Stop as we are getting the same result.

In order to have 3.3 V across the 4 series-connected diodes, each diode drop must be 0.825 V. Applying this voltage to the diode gives current  $I_D = 20.1$  mA. We can then find the resistor value using

#### 4.38 Constant voltage drop model:

$$\text{Using } v_D = 0.6 \text{ V}, \Rightarrow i_{D2} = \frac{V - 0.6}{R}$$

$$\Rightarrow i_{D2} = 1.01 i_{D1}$$

$$V - 0.6 = 1.01(V - 0.7)$$

$$V = 10.7 \text{ V}$$

For  $V = 3 \text{ V}$  and  $R = 1 \text{ k}\Omega$ :

$$\text{At } V_D = 0.6 \text{ V, } i_{D2} = \frac{3 - 0.6}{1} = 2.4 \text{ mA}$$

$$\frac{i_{D2}}{i_{D1}} = \frac{2.4}{2.3} = 1.04$$

Thus the percentage difference is 4%.

$$= \frac{1.3}{2} = 0.65 \text{ V. Using}$$

$$I_2 = I_1 e^{(V_2 - V_1)/V_T}$$

$$= 2e^{(0.65-0.7)/0.025}$$

$$= 0.2707 \text{ mA}$$

Thus current through each branch is 0.2707 mA.

The 1 mA will split in  $= \frac{1}{0.2707} = 3.69$  branches.

Choose  $N = 4$ .

There are 4 pairs of diodes in parallel.

∴ We need 8 diodes.

Current through each pair of diodes

$$= \frac{1 \text{ mA}}{4} = 0.25 \text{ mA}$$

$\therefore$  Voltage across each pair


$$= 2 \left[ 0.7 + 0.025 \ln \left( \frac{0.25}{2} \right) \right]$$

$$= 1.296 \text{ V}$$

**SPECIAL NOTE:** There is another possible design utilizing only 6 diodes and realizing a voltage of 1.313 V. It consists of the series connection of 4 parallel diodes and 2 parallel diodes.

**4.40** Refer to Example 4.2.

(a)

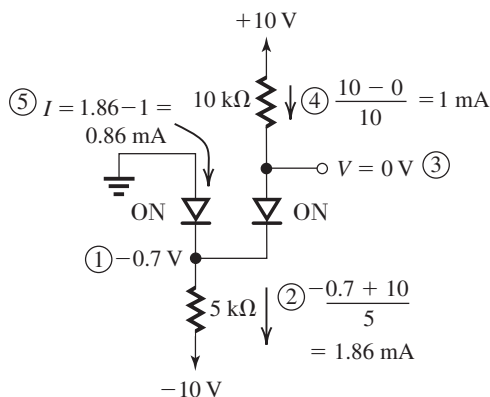

$$\frac{i_{D2}}{i_{D1}} = e^{5/25} = 1.221$$

% change

$$= \frac{i_{D2} - i_{D1}}{i_{D1}} \times 100 = \frac{1.221 - 1}{1} \times 100 = 22.1\%$$

For  $-5$  mV change we obtain

$$\frac{i_{D2}}{i_{D1}} = e^{-5/25} = 0.818$$

$$\% \text{ change} = \frac{i_{D2} - i_{D1}}{i_{D1}} \times 100 = \frac{0.818 - 1}{1} \times 100 = -18.1\%$$

Maximum allowable voltage signal change when the current change is limited to  $\pm 10\%$  is found as follows:

The current varies from 0.9 to 1.1


$$\frac{i_{D2}}{i_{D1}} = e^{\Delta V / V_T}$$

For 0.9,  $\Delta V = 25 \ln(0.9) = -2.63$  mV

For 1.1,  $\Delta V = 25 \ln(1.1) = +2.38$  mV

For  $\pm 10\%$  current change the voltage signal change is from  $-2.63$  mV to  $+2.38$  mV

**4.47**

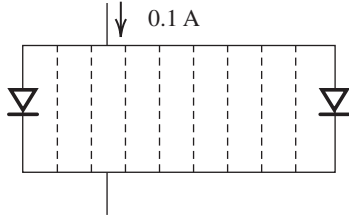

Ten diode connected in parallel and fed with a total current of 0.1 A. So the current through each diode =  $\frac{0.1}{10} = 0.01$  A

Small signal resistance of each diode

$$= \frac{V_T}{i_D} = \frac{25 \text{ mV}}{0.01 \text{ A}} = 2.5 \Omega$$

Equivalent resistance,  $R_{eq}$ , of 10 diodes connected in parallel is given by

$$R_{eq} = \frac{2.5}{10} = 0.25 \Omega$$

If there is one diode conducting 0.1 A current, then the small signal resistance of this diode

$$= \frac{25 \text{ mV}}{0.1 \text{ A}} = 0.25 \Omega$$

This value is the same as of 10 diodes connected in parallel.


If  $0.2 \Omega$  is the resistance for making connection, the resistance in each branch  
 $= r_d + 0.2 = 2.5 + 0.2 = 2.7 \Omega$

For a parallel combination of 10 diodes, equivalent resistance,  $R_{eq}$ , is

$$R_{eq} = \frac{2.7}{10} = 0.27 \Omega$$

If there is a single diode conducting all the 0.1 A current, the connection resistance needed for the single diode will be  $= 0.27 - 0.25 = 0.02 \Omega$ .

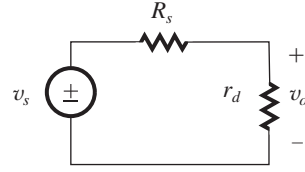**4.48** The dc current  $I$  flows through the diode giving rise to the diode resistance  $r_d = \frac{V_T}{I}$  and the small-signal equivalent circuit is represented by



$$v_o = v_s \times \frac{r_d}{r_d + R_s} = v_s \times \frac{V_T/I}{\frac{V_T}{I} + R_s} = v_s \times \frac{V_T}{V_T + IR_s}$$

$$\text{Now, } v_o = 10 \text{ mV} \times \frac{25 \text{ mV}}{25 \text{ mV} + 10^3 I}$$

$I$	$v_o$
1 mA	0.24 mV
0.1 mA	2.0 mV
1 $\mu$ A	9.6 mV

$$\text{For } v_o = \frac{1}{2} v_s = v_s \times \frac{0.025}{0.025 + 10^3 I}$$

$$\Rightarrow I = 25 \mu\text{A}$$

**4.49** As shown in Problem 4.48,

$$\frac{v_o}{v_i} = \frac{V_T}{V_T + R_s I} = \frac{0.025}{0.025 + 10^4 I} \quad (1)$$

Here  $R_s = 10 \text{ k}\Omega$

The current changes are limited  $\pm 10\%$ . Using exponential model, we get

$$\frac{i_{D2}}{i_{D1}} = e^{\Delta v / V_T} = 0.9 \text{ to } 1.1$$

$$\Delta v = 25 \times 10^{-3} \ln\left(\frac{i_{D2}}{i_{D1}}\right) \text{ and here}$$

For 0.9,  $\Delta v = -2.63$  mV

For 1.1,  $\Delta v = 2.38$  mV

The variation is  $-2.63$  mV to  $2.38$  mV for  $\pm 10\%$  current variation. Thus the largest symmetrical output signal allowed is  $2.38$  mV in amplitude. To

At  $I_Z = 2I_{ZT} = 0.01$  A,

$$V_Z = 17.6 + 0.01 \times 80 = 18.4 \text{ V}$$

$$P = 18.4 \times 0.01 = 0.184 \text{ W} = 184 \text{ mW}$$

(e)  $7.5 = V_{Z0} + 0.2 \times 1.5$

$$\Rightarrow V_{Z0} = 7.2 \text{ V}$$

At  $I_Z = 2I_{ZT} = 0.4$  A,

$$V_Z = 7.2 + 0.4 \times 1.5 = 7.8 \text{ V}$$

$$P = 7.8 \times 0.4 = 3.12 \text{ W}$$


**4.60** (a) Three 6.8-V zeners provide  $3 \times 6.8 = 20.4$  V with  $3 \times 10 = 30$ - $\Omega$  resistance. Neglecting  $R$ , we have

$$\text{Load regulation} = -30 \text{ mV/mA.}$$

(b) For 5.1-V zeners we use 4 diodes to provide 20.4 V with  $4 \times 30 = 120$ - $\Omega$  resistance.

$$\text{Load regulation} = -120 \text{ mV/mA}$$

**4.61**

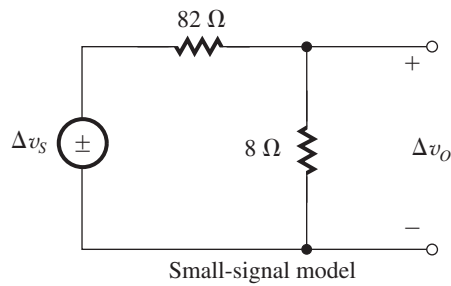

From the small-signal model we obtain

$$\frac{\Delta v_O}{\Delta v_S} = \frac{8}{8 + 82} = \frac{8}{90}$$

Now  $\Delta v_S = 1.0$  V.

$$\therefore \Delta v_O = \frac{8}{90} \Delta v_S = \frac{8}{90} \times 1.0$$

$$= 88.9 \text{ mV}$$

**4.62**  $V_Z = V_{Z0} + I_{ZT} r_Z$

$$9.1 = V_{Z0} + 0.02 \times 10$$

$$\Rightarrow V_{Z0} = 8.9 \text{ V}$$


At  $I_Z = 10$  mA,

$$V_Z = 8.9 + 0.01 \times 10 = 9.0 \text{ V}$$


At  $I_Z = 50$  mA,

$$V_Z = 8.9 + 0.05 \times 10 = 9.4 \text{ V}$$


**4.63**

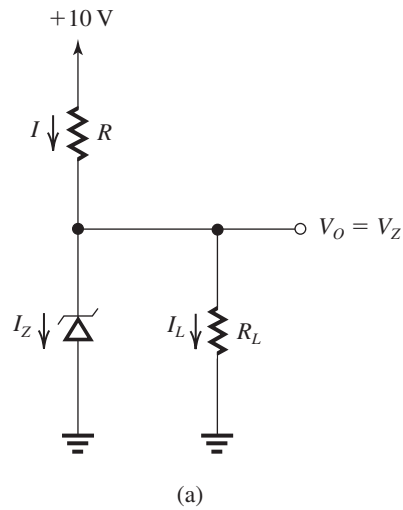

(a)

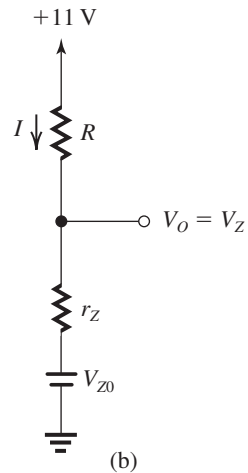

(b)

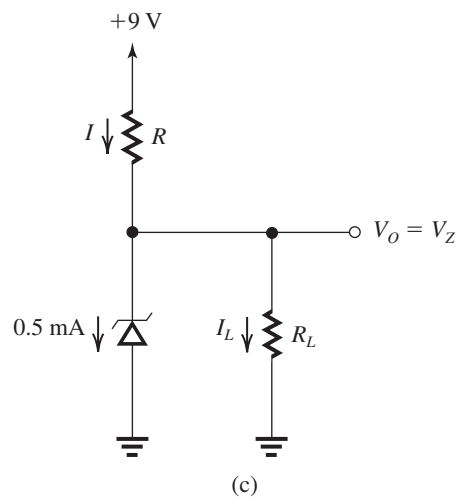

(c)