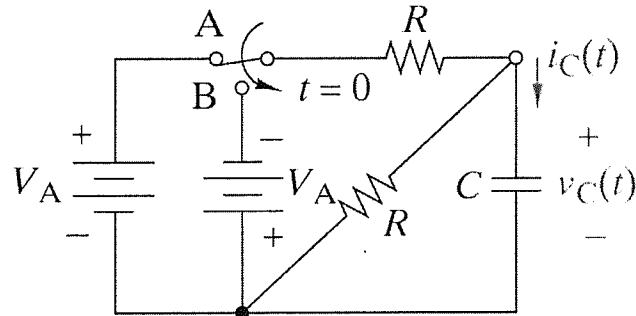


ECE332 Quiz 4


(10 minutes)

Name: Solution

1. [75 pts] **Given:** The switch below has been in position A for a long time.



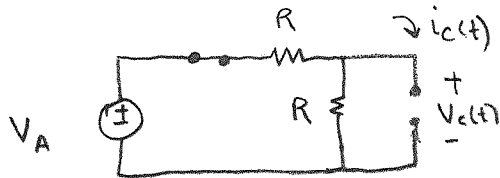
- a. [25 pts] **Find:** The initial values of the variables $i_C(t)$ and $v_C(t)$.



$$v_C(0) = V_A \frac{R}{R+R} = V_A/2$$

$$i_C(0) = 0$$

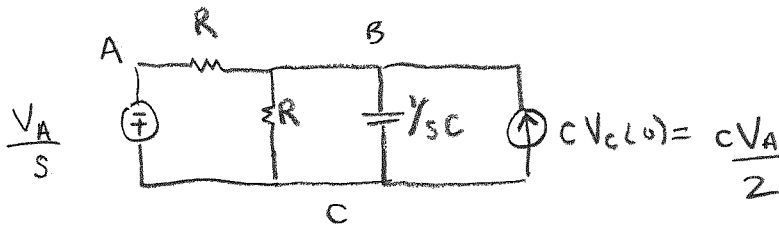- b. [25 pts] **Find:** Transform and redraw the circuit in the s domain for $t \geq 0$. Use **current sources** to represent initial conditions.




- c. [25 pts] **Find:** Write a set of node voltage equations to sufficient to determine the voltage drop across the top resistor. **Do not solve** for the node voltages.

$$A: \quad V_A = -\frac{V_A}{s}$$


$$B: \quad \frac{V_B - (-V_A/s)}{R} + \frac{V_B}{1/sC} + \frac{V_B}{R} - C V_C(0) = 0$$

$$C: \quad V_C = 0$$

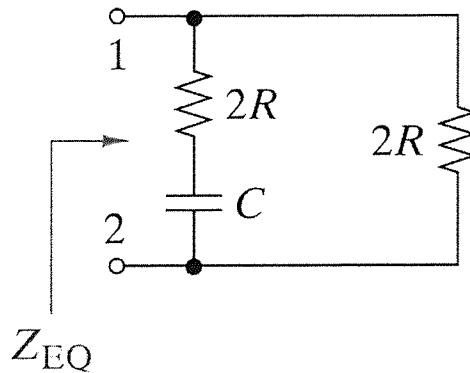2. [20 pts] **Given:** The circuit below in the zero state.



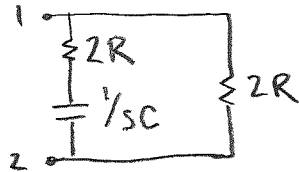a. [10 pts] **Find:** Transform and redraw the circuit in the s domain.



b. [10 pts] **Find:** The equivalent impedance Z_{EQ} . What are the poles ^{and zeroes} of the circuit?

$$\begin{aligned}
 & (2R + 1/sC) \parallel 2R \\
 = & \frac{(2R + 1/sC)(2R)}{2R + 1/sC + 2R} = \frac{4R^2 + 2R/sC}{4R + 1/sC} \quad \frac{sC}{sC} \\
 = & \frac{4R^2Cs + 2R}{4RCs + 1} \\
 = & \frac{4RC}{4RC} \cdot \frac{Rs + 1/2C}{s + 1/4RC} = \boxed{R \frac{s + 1/2RC}{s + 1/4RC}}
 \end{aligned}$$

zero $s = -1/2RC$

pole $s = -1/4RC$