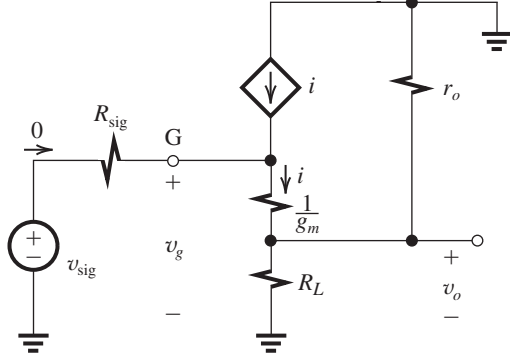


7.90



$$v_g = v_{\text{sig}}$$

Noting that r_o appears in effect in parallel with R_L , v_o is obtained as the ratio of the voltage divider formed by $(1/g_m)$ and $(R_L \parallel r_o)$,

$$G_v = \frac{v_o}{v_{\text{sig}}} = \frac{v_o}{v_g} = \frac{(R_L \parallel r_o)}{(R_L \parallel r_o) + \frac{1}{g_m}} \quad \text{Q.E.D.}$$

With R_L removed,

$$G_v = \frac{r_o}{r_o + \frac{1}{g_m}} = 0.98 \quad (1)$$

With $R_L = 500 \, \Omega$,

$$G_v = \frac{(500 \parallel r_o)}{(500 \parallel r_o) + \frac{1}{g_m}} = 0.49 \quad (2)$$

From Eq. (1), we have

$$\frac{1}{g_m} = \frac{r_o}{49}$$

Substituting in Eq. (2) and solving for r_o gives

$$r_o = 25,000 \, \Omega = 25 \, \text{k}\Omega$$

Thus

$$\frac{1}{g_m} = \frac{25,000}{49} \, \Omega$$

$$\Rightarrow g_m = 1.96 \, \text{mA/V}$$

7.91 Adapting Eq. (7.114) gives

$$\begin{aligned} G_v &= -\beta \frac{R_C \parallel R_L \parallel r_o}{R_{\text{sig}} + (\beta + 1)r_e} \\ &= -\frac{R_C \parallel R_L \parallel r_o}{\frac{R_{\text{sig}}}{\beta} + \frac{\beta + 1}{\beta} r_e} \\ &= -\frac{R_C \parallel R_L \parallel r_o}{\frac{R_{\text{sig}}}{\beta} + \frac{1}{g_m}} \end{aligned}$$

Thus,

$$|G_v| = \frac{10 \parallel r_o}{0.1 + \frac{1}{g_m}} \quad (1)$$

where r_o and $\frac{1}{g_m}$ are in kilohms and are given by

$$r_o = \frac{V_A}{I_C} = \frac{25 \, \text{V}}{I_C \, \text{mA}} \quad (2)$$

$$\frac{1}{g_m} = \frac{V_T}{I_C} = \frac{0.025 \, \text{V}}{I_C \, \text{mA}} \quad (3)$$


I_C (mA)	$1/g_m$ (k Ω)	r_o (k Ω)	$ G_v $ (V/V)
0.1	0.250	250	27.5
0.2	0.125	125	41.2
0.5	0.050	50	55.6
1.0	0.025	25	57.1
1.25	0.020	20	55.6

Observe that initially $|G_v|$ increases as I_C is increased. However, above about 1 mA this trend reverses because of the effect of r_o . From the table we see that gain of 50 is obtained for I_C between 0.2 and 0.5 mA and also for I_C above 1.25 mA. Practically speaking, one normally uses the low value to minimize power dissipation. The required value of I_C is found by substituting for r_o and $1/g_m$ from Eqs. (2) and (3), respectively, in Eq. (1) and equating G_v to 50. The result (after some manipulations) is the quadratic equation.

$$I_C^2 - 2.25I_C + 0.625 = 0$$

The two roots of this equation are $I_C = 0.325 \, \text{mA}$ and $1.925 \, \text{mA}$; our preferred choice is $I_C = 0.325 \, \text{mA}$.

7.92

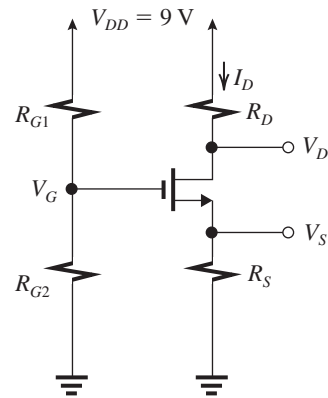

$$I_D = 1 \text{ mA}$$

$$I_D = \frac{1}{2} k_n V_{OV}^2$$

$$1 = \frac{1}{2} \times 2 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 1 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 1 + 1 = 2 \text{ V}$$

$$\text{Now, selecting } V_S = \frac{V_{DD}}{3} = 3 \text{ V}$$

$$I_D R_S = 3$$

$$R_S = \frac{3}{1} = 3 \text{ k}\Omega$$

Also,

$$I_D R_D = \frac{V_{DD}}{3} = 3 \text{ V}$$

$$\Rightarrow R_D = \frac{3}{1} = 3 \text{ k}\Omega$$

$$V_G = V_S + V_{GS}$$

$$= 3 + 2 = 5 \text{ V}$$

Thus the voltage drop across R_{G2} (5 V) is larger than that across R_{G1} (4 V). So we select

$$R_{G2} = 22 \text{ M}\Omega$$

and determine R_{G1} from

$$\frac{R_{G1}}{R_{G2}} = \frac{4 \text{ V}}{5 \text{ V}}$$

$$\Rightarrow R_{G1} = 0.8 R_{G2} = 0.8 \times 22$$

$$= 17.6 \text{ M}\Omega$$

Using only two significant figures, we have

$$R_{G1} = 18 \text{ M}\Omega$$


Note that this will cause V_G to deviate slightly from the required value of 5 V. Specifically,

$$V_G = V_{DD} \frac{R_{G2}}{R_{G2} + R_{G1}}$$

$$= 9 \times \frac{22}{22 + 18} = 4.95 \text{ V}$$

It can be shown (after simple but somewhat tedious analysis) that the resulting I_D will be $I_D = 0.986 \text{ mA}$, which is sufficiently close to the desired 1 mA. Since $V_D = V_{DD} - I_D R_D \simeq +6 \text{ V}$ and $V_G \simeq 5 \text{ V}$, and the drain voltage can go down to $V_G - V_t = 4 \text{ V}$, the drain voltage is 2 V above the value that causes the MOSFET to leave the saturation region.

7.93

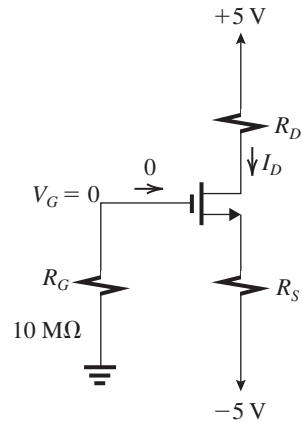

For $I_D = 0.5 \text{ mA}$

$$0.5 = \frac{1}{2} k_n V_{OV}^2$$

$$= \frac{1}{2} \times 1 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 1 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 1 + 1 = 2 \text{ V}$$

Since

$$V_G = 0 \text{ V}, \quad V_S = -V_{GS} = -2 \text{ V}$$

which leads to

$$R_S = \frac{V_S - (-5)}{I_C} = \frac{-2 + 5}{0.5} = 6 \text{ k}\Omega$$


V_D is required to be halfway between cutoff (+5 V) and saturation ($0 - V_t = -1 \text{ V}$). Thus

$$V_D = +2 \text{ V}$$

and

$$R_D = \frac{5 - 2}{0.5} = 6 \text{ k}\Omega$$

7.94

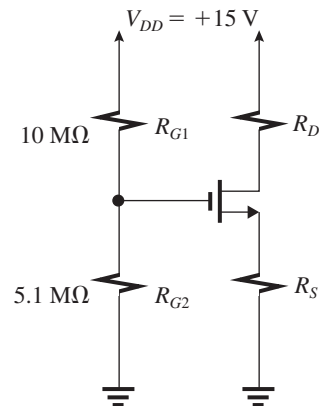

$$V_{GS} = V_{DD} - I_D R_D$$

$$= 10 - 10I_D$$

$$(a) V_t = 1 \text{ V and } k_n = 0.5 \text{ mA/V}^2$$

$$I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} \times 0.5 (10 - 10I_D - 1)^2$$

$$\Rightarrow I_D^2 - 1.84I_D + 0.81 = 0$$

$$I_D = 1.11 \text{ mA or } 0.73 \text{ mA}$$

The first root results in $V_D = -0.11 \text{ V}$, which is physically meaningless. Thus

$$I_D = 0.73 \text{ mA}$$

$$V_G = V_D = 10 - 10 \times 0.73 = 2.7 \text{ V}$$

$$(b) V_t = 2 \text{ V and } k_n = 1.25 \text{ mA/V}^2$$

$$I_D = \frac{1}{2} \times 1.25 (10 - 10I_D - 2)^2$$

$$\Rightarrow I_D^2 - 1.616I_D + 0.64 = 0$$


$$I_D = 0.92 \text{ mA or } 0.695 \text{ mA}$$

The first root can be shown to be physically meaningless, thus

$$I_D = 0.695 \text{ mA}$$

$$V_G = V_D = 10 - 10 \times 0.695 = 3.05 \text{ V}$$

7.102

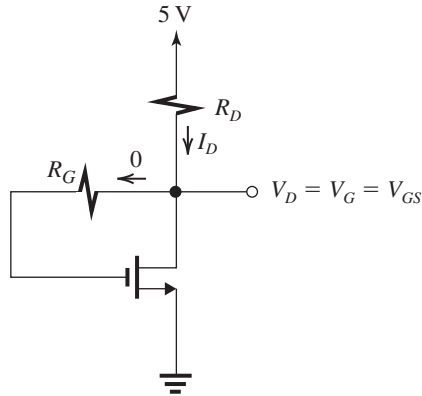


$$I_D = 0.2 = \frac{1}{2} \times 10 (V_{GS} - V_t)^2$$

$$\Rightarrow V_{GS} = 1.2 \text{ V}$$

$$R_D = \frac{5 - 1.2}{0.2} = 19 \text{ k}\Omega$$

7.103

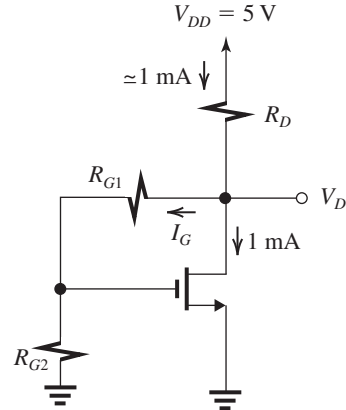

$$I_D = \frac{1}{2} k_n V_{OV}^2$$

$$1 = \frac{1}{2} \times 8 V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.5 \text{ V}$$

Since the transistor leaves the saturation region of operation when $v_D < V_{OV}$, we select

$$V_D = V_{OV} + 2$$

$$V_D = 2.5 \text{ V}$$

Since $I_G \ll I_D$, we can write

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{5 - 2.5}{1} = 2.5 \text{ k}\Omega$$

$$V_{GS} = V_t + V_{OV} = 0.8 + 0.5 = 1.3 \text{ V}$$

Thus the voltage drop across R_{G2} is 1.3 V and that across R_{G1} is $(2.5 - 1.3) = 1.2 \text{ V}$. Thus R_{G2} is the larger of the two resistances, and we select $R_{G2} = 22 \text{ M}\Omega$ and find R_{G1} from

$$\frac{R_{G1}}{R_{G2}} = \frac{1.2}{1.3} \Rightarrow R_{G1} = 20.3 \text{ M}\Omega$$

Specifying all resistors to two significant digits, we have $R_D = 2.5 \text{ k}\Omega$, $R_{G1} = 22 \text{ M}\Omega$, and $R_{G2} = 20 \text{ M}\Omega$.

$$7.104 \quad \frac{R_{B1}}{R_{B1} + R_{B2}} \times 3 = 0.710$$

$$\Rightarrow \frac{R_{B2}}{R_{B1}} = 3.225$$

Given that R_{B1} and R_{B2} are 1% resistors, the maximum and minimum values of the ratio R_{B2}/R_{B1} will be $3.225 \times 1.02 = 3.2895$ and $3.225 \times 0.98 = 3.1605$. The resulting V_{BE} will be 0.699 V and 0.721 V, respectively.

Correspondingly, I_C will be

Thus,

$$R_1 = R_2 = R_E \left(\frac{V_{CC} - 2V_{BE}}{V_{CC}} \right)$$

For $V_{CC} = 10 \text{ V}$ and $V_{BE} = 0.7 \text{ V}$,

$$R_1 = R_2 = R_E \left(\frac{10 - 1.4}{10} \right) = 0.86 R_E$$


To obtain $I_O = 0.5 \text{ mA}$,

$$0.5 = \frac{V_{CC}}{2R_E} = \frac{10}{2R_E}$$

$$\Rightarrow R_E = 10 \text{ k}\Omega$$

$$R_1 = R_2 = 8.6 \text{ k}\Omega$$

7.116

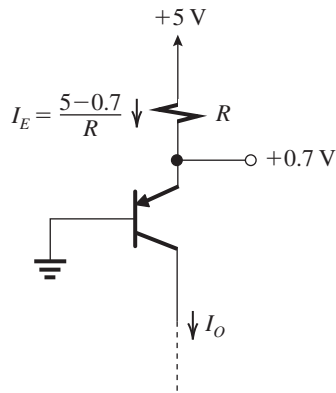

$$I_O = \alpha I_E \simeq 0.5 \text{ mA}$$

$$I_E = 0.5 \text{ mA}$$

$$\Rightarrow R = \frac{5 - 0.7}{0.5} = 8.6 \text{ k}\Omega$$

$$v_{C\max} = 0.7 - V_{EC\text{sat}} = 0.7 - 0.3$$

$$= +0.4 \text{ V}$$

This figure belongs to Problem 7.118.

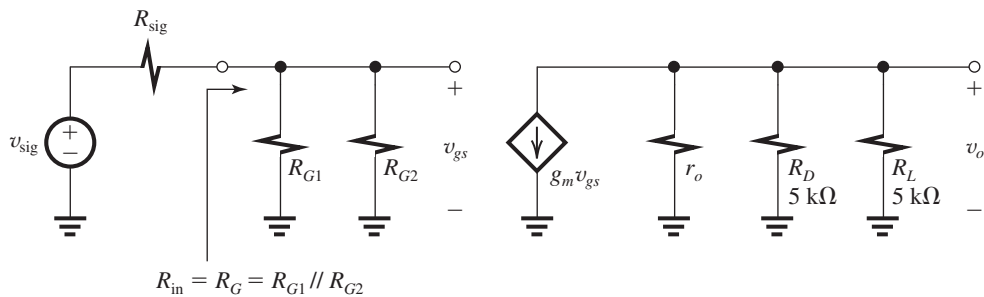


Figure 2

7.117 Refer to the equivalent circuit in Fig. 7.55(b).

$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_D \parallel R_L \parallel r_o)$$

$$= -\frac{R_G}{R_G + R_{sig}} g_m (R_D \parallel R_L \parallel r_o)$$

$$= -\frac{10}{10 + 1} \times 3 \times (10 \parallel 20 \parallel 100)$$

$$= -17 \text{ V/V}$$

7.118 (a) Refer to Fig. P7.118. The dc circuit can be obtained by opening all coupling and bypass capacitors, resulting in the circuit shown in Fig. 1.

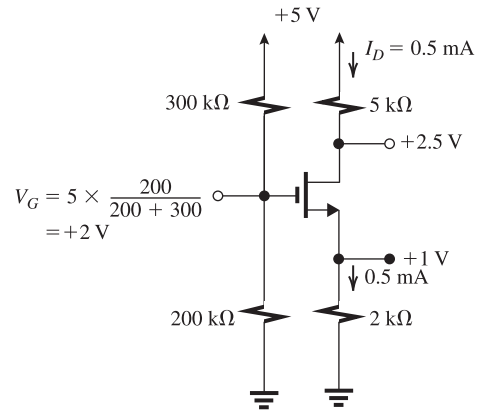


Figure 1

See analysis on figure.

$$V_{GS} = 2 - 1 = 1 \text{ V}$$

$$V_{OV} = V_{GS} - V_t = 1 - 0.7 = 0.3 \text{ V}$$

Since V_D at 2.5 V is 1.2 V higher than $V_S + V_{OV} = 1 + 0.3 = 1.3 \text{ V}$, the transistor is

indeed operating in saturation. (Equivalent $V_D = 2.5$ V is higher than $V_G - V_t = 1.3$ V by 1.2 V.)

$$I_D = \frac{1}{2} k_n V_{OV}^2$$

$$0.5 = \frac{1}{2} k_n \times 0.3^2$$

$$\Rightarrow k_n = 11.1 \text{ mA/V}^2$$

(b) The amplifier small-signal equivalent-circuit model is shown in Fig. 2.

$$R_{in} = R_{G1} \parallel R_{G2} = 300 \text{ k}\Omega \parallel 200 \text{ k}\Omega = 120 \text{ k}\Omega$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.5}{0.3} = 3.33 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{50}{0.5} = 100 \text{ k}\Omega$$

$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (r_o \parallel R_D \parallel R_L)$$

$$= -\frac{120}{120 + 120} \times 3.33 \times (100 \parallel 5 \parallel 5)$$

$$= -4.1 \text{ V/V}$$

$$(c) V_G = 2 \text{ V}, \quad V_D = 2.5 \text{ V}$$

$$\hat{v}_{GS} = 2 + \hat{v}_{gs}, \quad \hat{v}_{DS} = 2.5 - |A_v| \hat{v}_{gs}$$

where

$$|A_v| = g_m (r_o \parallel R_D \parallel R_L) = 8.1 \text{ V/V}$$

To remain in saturation,

$$\hat{v}_{DS} \geq \hat{v}_{GS} - V_t$$

$$2.5 - 8.1 \hat{v}_{gs} \geq 2 + \hat{v}_{gs} - 0.7$$

This is satisfied with equality at

$$\hat{v}_{gs} = \frac{2.5 - 1.3}{9.1} = 0.132 \text{ V}$$

The corresponding value of \hat{v}_{sig} is

$$\hat{v}_{sig} = \hat{v}_{gs} \left(\frac{120 + 120}{120} \right) = 2 \times 0.132 = 0.264 \text{ V}$$

The corresponding amplitude at the output will be

$$|G_v| \hat{v}_{sig} = 4.1 \times 0.264 = 1.08 \text{ V}$$

(d) To be able to double \hat{v}_{sig} without leaving saturation, we must reduce \hat{v}_{gs} to half of what would be its new value; that is, we must keep \hat{v}_{gs} unchanged. This in turn can be achieved by connecting an unbypassed R_s equal to $1/g_m$,

$$R_s = \frac{1}{3.33 \text{ mA/V}} = 300 \text{ }\Omega$$

Since \hat{v}_{gs} does not change, the output voltage also will not change, thus $\hat{v}_o = 1.08$ V.

7.119 Refer to Fig. P7.119.

(a) DC bias:

$$|V_{OV}| = 0.3 \text{ V} \Rightarrow V_{SG} = |V_{tp}| + |V_{OV}| = 1 \text{ V}$$

Since $V_G = 0$ V, $V_S = V_{SG} = +1$ V, and

$$I_D = \frac{2.5 - 1}{R_S} = 0.3 \text{ mA}$$

$$\Rightarrow R_S = \frac{1.5}{0.3} = 5 \text{ k}\Omega$$

$$(b) G_v = -g_m R_D$$

where

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.3}{0.3} = 2 \text{ mA/V}$$

Thus,

$$-10 = -2R_D \Rightarrow R_D = 5 \text{ k}\Omega$$

$$(c) v_G = 0 \text{ V (dc)} + v_{sig}$$

$$v_{Gmin} = -\hat{v}_{sig}$$

$$\hat{v}_D = V_D + |G_v| \hat{v}_{sig}$$

where

$$V_D = -2.5 + I_D R_D = -2.5 + 0.3 \times 5 = -1 \text{ V}$$

To remain in saturation,

$$\hat{v}_D \leq \hat{v}_G + |V_{tp}|$$

$$-1 + 10 \hat{v}_{sig} \leq -\hat{v}_{sig} + 0.7$$

Satisfying this constraint with equality gives

$$\hat{v}_{sig} = 0.154 \text{ V}$$

and the corresponding output voltage

$$\hat{v}_d = |G_v| \hat{v}_{sig} = 1.54 \text{ V}$$

$$(d) \text{ If } \hat{v}_{sig} = 50 \text{ mV, then}$$

$$V_D + |G_v| \hat{v}_{sig} = -\hat{v}_{sig} + |V_{tp}|$$

where

$$V_D = -2.5 + I_D R_D = -2.5 + 0.3 R_D$$

and

$$|G_v| = g_m R_D = 2R_D$$

Thus

$$-2.5 + 0.3 R_D + 2R_D \hat{v}_{sig} = -\hat{v}_{sig} + |V_{tp}|$$

$$-2.5 + 0.3 R_D + 2R_D \times 0.05 = -0.05 + 0.7$$

$$0.4 R_D = 3.15$$

$$\Rightarrow R_D = 7.875 \text{ k}\Omega$$

$$G_v = -g_m R_D = -2 \times 7.875 = -15.75 \text{ V/V}$$

7.120 Refer to Fig. P7.120.

$$R_{i2} = \frac{1}{g_{m2}} = 50 \, \Omega$$

$$\Rightarrow g_{m2} = \frac{1}{50} \, \text{A/V} = 20 \, \text{mA/V}$$

If Q_1 is biased at the same point as Q_2 , then

$$g_{m1} = g_{m2} = 20 \, \text{mA/V}$$

$$i_{d1} = g_{m1} \times 5 \, (\text{mV})$$

$$= 20 \times 0.005 = 0.1 \, \text{mA}$$

$$v_{d1} = i_{d1} \times 50 \, \Omega$$

$$= 0.1 \times 50 = 5 \, \text{mV}$$

$$v_o = i_{d1} R_D = 1 \, \text{V}$$

$$R_D = \frac{1 \, \text{V}}{0.1 \, \text{mA}} = 10 \, \text{k}\Omega$$

7.121 (a) DC bias: Refer to the circuit in Fig. P7.121 with all capacitors eliminated:

$$R_{\text{in at gate}} = R_G = 10 \, \text{M}\Omega$$

$V_G = 0$, thus $V_S = -V_{GS}$, where V_{GS} can be obtained from

$$I_D = \frac{1}{2} k_n V_{OV}^2$$

$$0.4 = \frac{1}{2} \times 5 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.4 \, \text{V}$$

$$V_{GS} = V_t + 0.4 = 0.8 + 0.4 = 1.2 \, \text{V}$$

$$V_S = -1.2 \, \text{V}$$

$$R_S = \frac{-1.2 - (-5)}{0.4} = 9.5 \, \text{k}\Omega$$

To remain in saturation, the minimum drain voltage must be limited to $V_G - V_t = 0 - 0.8 = -0.8 \, \text{V}$. Now, to allow for 0.8-V negative signal swing, we must have

$$V_D = 0 \, \text{V}$$

and

$$R_D = \frac{5 - 0}{0.4} = 12.5 \, \text{k}\Omega$$

$$(b) \, g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.4}{0.4} = 2 \, \text{mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{40}{0.4} = 100 \, \text{k}\Omega$$

(c) If terminal Z is connected to ground, the circuit becomes a CS amplifier,

$$G_v = -\frac{v_y}{v_{\text{sig}}} = \frac{R_G}{R_G + R_{\text{sig}}} \times -g_m(r_o \parallel R_D \parallel R_L)$$

$$= -\frac{10}{10 + 1} \times 2 \times (100 \parallel 12.5 \parallel 10) \\ = -9.6 \, \text{V/V}$$


(d) If terminal Y is grounded, the circuit becomes a CD or source-follower amplifier:

$$\frac{v_z}{v_x} = \frac{(R_S \parallel r_o)}{(R_S \parallel r_o) + \frac{1}{g_m}} \\ = \frac{(9.5 \parallel 100)}{(9.5 \parallel 100) + \frac{1}{2}} = 0.946 \, \text{V/V}$$

Looking into terminal Z, we see R_o :

$$R_o = R_S \parallel r_o \parallel \frac{1}{g_m} \\ = 9.5 \parallel 100 \parallel \frac{1}{2} = 473 \, \Omega$$

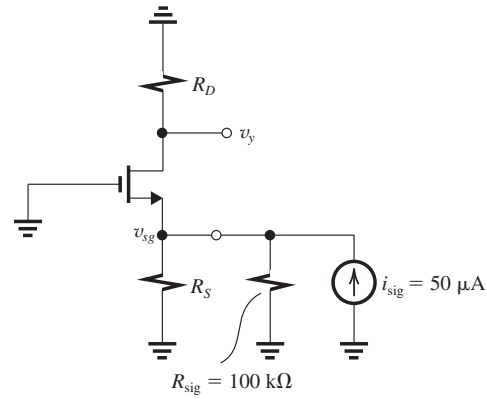(e) If X is grounded, the circuit becomes a CG amplifier.



The figure shows the circuit prepared for signal calculations.

$$v_{sg} = i_{\text{sig}} \times \left[R_{\text{sig}} \parallel R_S \parallel \frac{1}{g_m} \right] \\ = 50 \times 10^{-3} (\text{mA}) \left[100 \parallel 9.5 \parallel \frac{1}{2} \right] (\text{k}\Omega) \\ = 0.024 \, \text{V} \\ v_y = (g_m R_D) v_{sg} \\ = (2 \times 12.5) \times 0.024 = 0.6 \, \text{V}$$

7.122 (a) Refer to the circuit of Fig. P7.122(a):

$$A_{vo} \equiv \frac{v_{o1}}{v_i} = \frac{10}{10 + \frac{1}{g_m}} = \frac{10}{10 + \frac{1}{10}} = 0.99 \, \text{V/V}$$

$$R_o = \frac{1}{g_m} \parallel 10 \, \text{k}\Omega = 0.1 \parallel 10 = 99 \, \Omega$$